

# Rectifiers and Other Diode Circuits

## Topics Discussed


- 1 Half-wave and full-wave rectifier circuits
- 2 Analysis of rectifiers
- 3 Filters
- 4 Clipping and clamping circuits

### 15.1 ► RECTIFIERS

#### 15.1.1 Introduction

A rectifier is a device that converts ac supply into dc using diodes. Rectification can be done by half-wave or full-wave rectification circuits. All electronic circuits need a low dc voltage for their operation. The supply voltage available is from the ac mains which is 230 V, 50 Hz supply. A rectifier will first step down the ac supply voltage to the required level by using a step-down transformer. A single diode can be used to rectify the ac voltage into half-wave rectified dc voltage. Since the rectified voltage is a unidirectionally changing dc, filter circuits are used to get steady dc output.

In this section we will discuss half-wave and full-wave rectifier circuits.

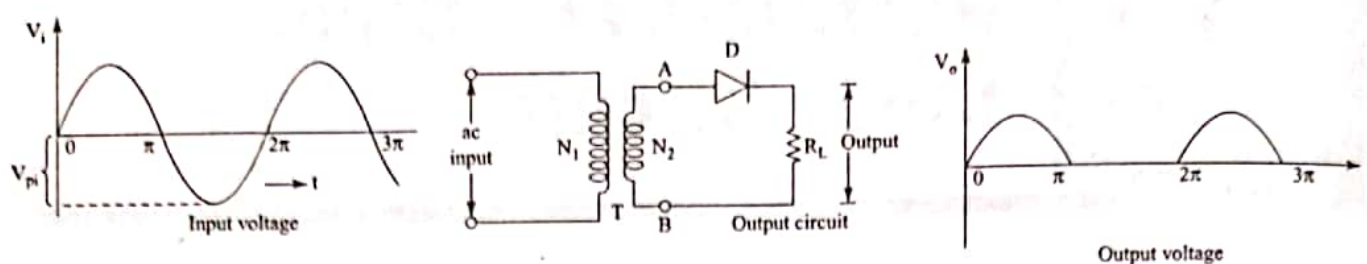**FIGURE 15.1**

Half-wave rectifier circuit with input and output voltage waveforms

### 15.1.2 Half-Wave Rectifier

A half-wave rectifier circuit consisting of a transformer, a diode, and a load represented by a resistor has been shown in Fig. 15.1. The input and output wave shapes have been shown. The diode is forward biased during the positive half cycle of the applied voltage and reverse biased during the negative half cycle.

During the positive half cycle, i.e., from time 0 to  $\pi$ , voltage is positive, and hence, terminal A of the transformer, T is positive. Diode is forward biased, and hence, current will flow through the diode and through the load resistance,  $R_L$ . If a step down transformer is used, the magnitude of output voltage will be reduced. If however, step down of voltage is not required, a transformer having an equal turn ratio, i.e.,  $N_2/N_1$  will be used. The function of the transformer will be to electrically isolate the dc output circuit from the input circuit.

During the negative half cycle of the input voltage wave, the terminal A of the transformer will be negative and terminal B will be positive. The diode will be reverse biased and virtually no current will flow through the diode and the load.


This sequence of allowing the positive half cycle of current through the diode and blocking the negative half cycle will continue for each and every cycle of power supply. As a result, a half-wave rectified current will flow through the output circuit. The voltage drop across the load resistance,  $R_L$  will be the output voltage,  $V_o$  which will be a half-wave rectified voltage. When the diode is reverse biased, the maximum or peak voltage of the negative half cycle of the input will be appearing across the diode terminals. This is the peak of the reverse voltage  $V_{pi}$  (see Fig. 15.1) or peak-inverse voltage (PIV) which is getting applied to the diode in every alternate half cycles.

It is seen that a diode works as a closed switch during the positive half cycle of the input voltage and works as an open switch during the negative half cycle. The output voltage appears across the load during the positive half cycle only. The load voltage and load current although positive all the time (i.e., unidirectional) are fluctuating dc as its magnitudes changing. Our aim will be to obtain steady dc at the output.

The average value of this fluctuating dc as also its RMS values can be calculated as  $I_m/\pi$  and  $I_m/2$ , respectively.

The performance parameters of a half-wave rectifier output are calculated in terms of the output dc current (i.e., the average value of the rectified wave), the RMS value of the output current, the output voltage, ripple factor, peak inverse voltage, etc.

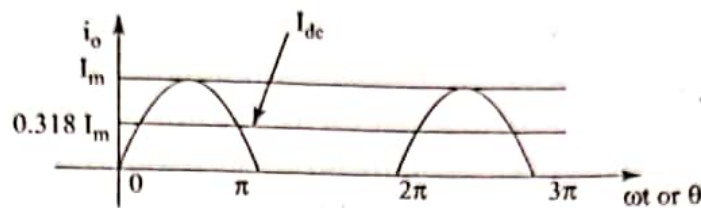

**FIGURE 15.2**

Half-wave rectified current

### 15.1.3 Analysis of Half-Wave Rectifier

The equation for a sinusoidal voltage is written as  $v = V_m \sin \theta$  and for a sinusoidal current,

$$i = I_m \sin \theta,$$

where  $i$  is the instantaneous value,  $I_m$  is the maximum value, and  $\theta = \omega t$ .

The average value is calculated by integrating the current for a period  $\theta = 0$  to  $\theta = \pi$  and averaging it for the entire cycle, i.e.,  $\theta = 0$  to  $\theta = 2\pi$ .

$I_{dc}$  is the average value of the rectified current.

$$\begin{aligned} I_{dc} = I_{av} &= \frac{1}{2\pi} \int_0^\pi i d\theta = \frac{1}{2\pi} \int_0^\pi I_m \sin \theta d\theta \\ &= \frac{I_m}{2\pi} [-\cos \theta]_0^\pi \\ &= \frac{I_m}{2\pi} [ -(-1) - (-1) ] \\ &= \frac{I_m}{\pi} = 0.318 I_m \end{aligned}$$

The RMS value,  $I$  is calculated by first squaring the current, then taking its mean, and then taking its root as

$$I = \sqrt{\frac{1}{2\pi} \int_0^\pi i^2 d\theta} \quad \text{or,} \quad I^2 = \frac{1}{2\pi} \int_0^\pi i^2 d\theta$$

$$I^2 = \frac{1}{2\pi} \int_0^\pi I_m^2 \sin^2 \theta d\theta$$

or,

$$I^2 = \frac{I_m^2}{2\pi} \int_0^\pi \left[ \frac{1 - \cos 2\theta}{2} \right] d\theta = \frac{I_m^2}{4\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^\pi$$

or,

$$= \frac{I_m^2}{4\pi} \left[ \pi - \frac{\sin 2\pi}{2} - \left( 0 - \frac{\sin 2 \times 0}{2} \right) \right]$$

$$= \frac{I_m^2}{4\pi} \times \pi$$

$$= \frac{I_m^2}{4}$$

or,

$$I_{rms} = \frac{I_m}{2}$$

Ripple Factor: The output of a half-wave rectifier is a pulsating dc. If we analyse, we will see that it has a steady dc component and an ac component. The ac component is called the ripple. Ripple factor is defined as the ratio of the RMS value of ac component to the value of dc component. The ripple factor indicates the level of fluctuation of the output voltage from its steady value. Ripple is an undesired effect and should be minimized. The ripple factor,  $r$  for a half-wave rectifier is calculated as

$$\text{Ripple Factor, } r = \frac{\text{RMS value of ac component}}{\text{value of dc component}} \\ = \frac{I_{ac}}{I_{dc}}$$

$$\text{Again, } I_{rms}^2 = I_{dc}^2 + I_1^2 + I_2^2 + I_4^2 + \dots = I_{dc}^2 + I_{ac}^2$$

where  $I_1, I_2, I_4$ , etc., are the fundamental and harmonics of the ac component

$$\text{or, } I_{rms} = \sqrt{I_{dc}^2 + I_{ac}^2}$$

$$\text{or, } I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

where  $I_{ac}$  is the RMS value of the ac component of the output current.

$I_{dc}$  is the dc component of the output current and  $I_{rms}$  is the RMS value of the output current.

Substituting

$$r = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

Considering  $I_{rms} = \frac{I_m}{2}$  and  $I_{dc} = \frac{I_m}{\pi}$  a half-wave rectifier,

$$r = \sqrt{\left[\frac{I_m/2}{I_m/\pi}\right]^2 - 1} \\ = \sqrt{\frac{\pi^2}{4} - 1} \\ = 1.21$$

ripple factor,

Output voltage,  $V_{dc}$  across the load is

$$V_{dc} = I_{dc} R_L = \frac{I_m}{\pi} R_L = \frac{V_m}{\pi} = 0.318 V_m$$

Rectifier efficiency: It is calculated as the ratio of output power to input power.

$$\text{DC output power, } P_{dc} = I_{dc}^2 R_L = \left(\frac{I_m}{\pi}\right)^2 R_L$$

$$\text{AC input power, } P_{ac} = \text{Power dissipated in diode junction} + \text{Power dissipated in the load} \\ = I_{rms}^2 R_f + I_{rms}^2 R_L$$

The forward resistance,  $R_f$  of the diode is very small, and hence,  $I_{rms}^2 R_f$  can be neglected in comparison with  $I_{rms}^2 R_L$ .



$$\begin{aligned}
 \text{Therefore, rectifier efficiency} &= \frac{P_{dc}}{P_{ac}} = \frac{I_m^2}{\pi^2} RL \div I_{rms}^2 R_L \\
 &= \frac{I_m^2 RL}{\pi^2 I_{rms}^2 RL} = \frac{I_m^2}{\pi^2 \cdot \left(\frac{I_m}{2}\right)^2} \\
 &= \frac{4}{\pi^2} = 0.406 = 40.6 \text{ per cent}
 \end{aligned}$$

This value of efficiency is considered low and ripple factor is considered very high. A filter circuit has to be used to minimize the ripples.

Peak inverse voltage (PIV): As mentioned earlier, PIV is the maximum value of reverse voltage that appears across the diode when it gets reverse biased. Here

$$PIV = V_m$$

Rectifier diodes are specified for their average forward current-carrying capacity and their reverse voltage capacity, i.e., their PIV capacity. For example, low-power rectifier diode series, IN 4000 to IN 4007 are rated for forward current of 1000 mA and maximum reverse voltage of value varying from 50 V to 1000 V.

Voltage Regulation of the rectifier is calculated using the relation,

$$\text{Voltage regulation} = \frac{V_{dc} \text{ at no load} - V_{dc} \text{ on full load}}{V_{dc} \text{ on full load}}$$

The difference between no-load voltage and full-load voltage is the voltage drop in the transformer winding and across the diode. The value of voltage regulation, which is generally expressed in percentage should be low.

### EXAMPLE 15.1

A half-wave diode rectifier has a forward voltage drop, i.e., voltage drop across the diode when conducting is 0.7 V. The load resistance is 600  $\Omega$ . The RMS value of the ac input is 28.87 V. Calculate  $I_{dc}$ ,  $I_{rms}$ , PIV, and form factor.

### SOLUTION


The half-wave rectifier circuit with the given data is shown in Fig. 15.3.

$$V_i(\text{RMS}) = 28.27 \text{ V}$$

$$\begin{aligned}
 V_i(\text{max}) &= \sqrt{2} V_i(\text{RMS}) \\
 &= 1.414 \times 28.27
 \end{aligned}$$

$$\text{i.e., } V_m = 40 \text{ V}$$

$$PIV = V_m = 40 \text{ V}$$

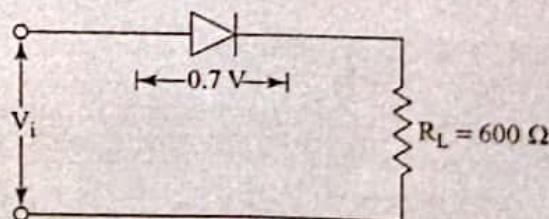

**FIGURE 15.3**

Half-wave rectifier circuit

$$I_{dc} = \frac{I_m}{\pi};$$

$$I_m = \frac{V_m - 0.7}{R_L} = \frac{40 - 0.7}{600} = \frac{39.3}{600} \text{ A}$$

$$I_{dc} = \frac{39.3}{600 \times \pi} = 0.0208 \text{ A} = 20.8 \text{ mA}$$

$$I_{rms} = \frac{I_m}{2} \frac{39.3}{600 \times 2} = 0.0327 \text{ A} = 32.7 \text{ mA}$$

$$\begin{aligned} \text{Form factor} &= \frac{\text{RMS value}}{\text{Average value}} = \frac{I_{rms}}{I_{dc}} = \frac{32.7}{20.8} \\ &= 1.57 \end{aligned}$$

### EXAMPLE 15.2

A half-wave rectifier produces a maximum load current (peak value) of 50 mA through a  $1200 \, \Omega$  resistor. Calculate the PIV of the diode. The diode is of silicon material.

#### SOLUTION

Assuming a voltage drop of 0.7 V across the silicon diode, the peak value of current,  $I_m$  is

$$I_m = \frac{V_m - 0.7}{R_L} = \frac{V_m - 0.7}{1200}$$

$I_m$  is given as 40 mA.

Therefore,

$$40 \times 10^{-3} = \frac{V_m - 0.7}{1200}$$

or,

$$V_m - 0.7 = 1200 \times 40 \times 10^{-3} = 48 \text{ V}$$

or,

$$V_m = 48 + 0.7 = 48.7 \text{ V}$$

$$\text{PIV} = V_m = 48.7 \text{ V}$$

### EXAMPLE 15.3

A half-wave rectifier circuit has been made using a step-down transformer of turn ratio 10:1. The input voltage is  $v = 325 \sin \omega t$  the diode forward resistance is  $25 \, \Omega$ . A load resistance of  $1.2 \text{ k}\Omega$  has been connected in the circuit. Assuming a secondary winding resistance of the transformer as  $1 \, \Omega$ , calculate the following: (a) RMS value of load current (b) rectification efficiency, and (c) ripple factor.



**SOLUTION**

Input voltage,  $v = 325 \sin \omega t$

Input,  $V_m = 325$

Transformer shown in Fig. 15.4, has a turn ratio of 10:1

The output  $V_m = \frac{325}{10} = 32.5 \text{ V}$

$$I_m = \frac{V_m}{R_2 + R_F + R_L}$$

where  $R_2$  is the secondary winding resistance,  $R_F$  is the forward resistance of the diode and  $R_L$  is the load resistance.

$$\begin{aligned} I_m &= \frac{32.5}{1 + 25 + 1200} \\ &= \frac{32.5}{1226} \text{ A} \\ &= 26.5 \text{ mA} \end{aligned}$$

Since it is a half-wave rectifier circuit,

$$I_{\text{rms}} = \frac{I_m}{2} = \frac{26.5}{2} = 13.25 \text{ mA}$$


$$I_{\text{dc}} = \frac{I_m}{\pi} = \frac{26.5}{3.14} = 8.44 \text{ mA}$$

$$\begin{aligned} \text{output dc power} &= I_{\text{dc}}^2 R_L = (8.44 \times 10^{-3})^2 \times 1200 \\ &= 85.48 \text{ mW} \end{aligned}$$

$$\begin{aligned} \text{AC input power} &= (I_{\text{rms}})^2 [R_2 + R_F + R_L] \\ &= (13.25 \times 10^{-3})^2 \times 1226 \\ &= 0.215 \text{ W} = 215 \text{ mW} \end{aligned}$$

$$\begin{aligned} \text{Rectifier efficiency} &= \frac{\text{Output dc power}}{\text{Input ac power}} \times 100 \\ &= \frac{85.48 \times 100}{215} = 39.75 \text{ per cent} \end{aligned}$$

$$\text{Ripple factor, } r = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{dc}}}\right)^2 - 1} = \sqrt{\left(\frac{13.25}{8.44}\right)^2 - 1} = 1.21$$

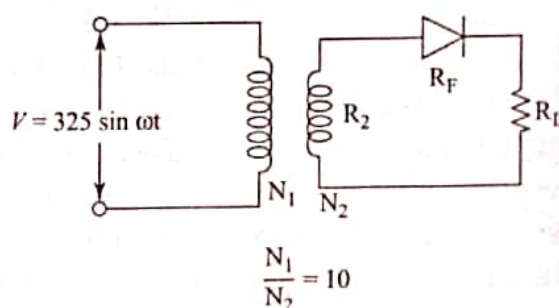

**FIGURE 15.4**


Half-wave rectifier

### 15.1.4 Full-Wave Rectifier

Full-wave rectifiers can be made using two diodes and a centre-tapped transformer. Full-wave rectifiers are also made using a two-winding transformer and four diodes. Such rectifiers are called bridge rectifiers. These are discussed as follows.

**Two-diode full-wave rectifier:** here ac input voltage is supplied from the secondary of a centre-tapped transformer. The circuit consists of the transformer, two diodes and the load resistance. The circuit is essentially the summation of two half-wave rectifiers as shown in Fig. 15.5.

For the positive half cycle of the input voltage, diode  $D_1$  will conduct. This is because terminal A is positive and the diode  $D_1$  is forward biased. As terminal B is negative, diode  $D_2$  will not conduct. In the negative half cycle, terminal B is positive and terminal A is negative. Hence, diode  $D_2$  will conduct and diode  $D_1$  will be reverse biased. This way in each half cycle one of the two diodes will conduct and current will flow through the load resistance,  $R_L$ . The output current and the output voltage across the load will be a full-wave rectified current and voltage, respectively. The output wave form is a series of consecutive positive half cycles of sinusoidal wave form. The current through the load resistance is unidirectional but its magnitude is fluctuating as shown in Fig. 15.5. The PIV is the maximum voltage that would appear across a diode when it is reverse biased. Here, when  $D_1$  is conducting,  $D_2$  is reverse biased and vice versa. When  $D_1$  is conducting, the voltage that would appear across diode  $D_2$  is the sum of the voltage across the lower half of the transformer secondary winding and the voltage appearing across the load. PIV of the diode is equal to  $2 V_m$ .

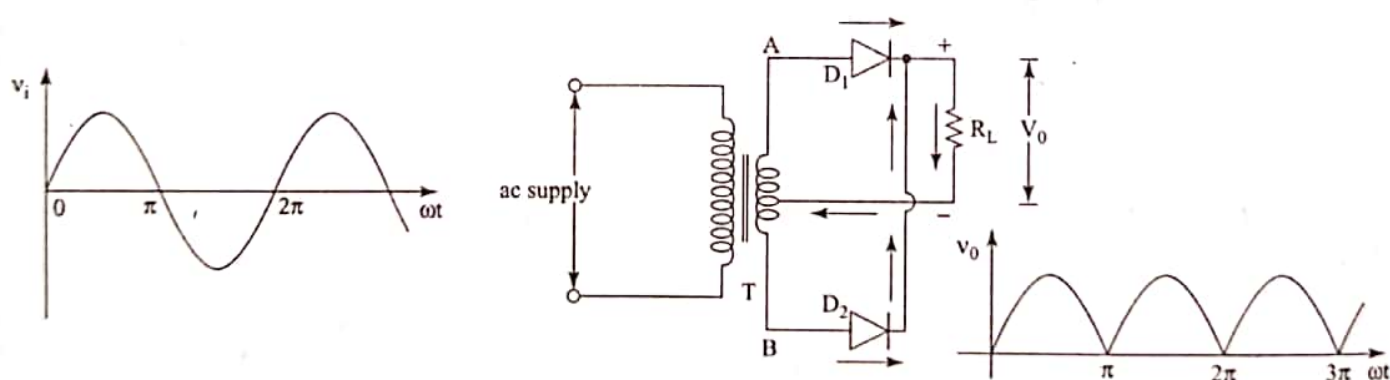

**FIGURE 15.5**

Full-wave rectifier using two diodes and a centre-tapped transformer

### 15.1.5 Full-Wave Bridge Rectifier

A bridge rectifier circuit uses four diodes connected in the form of a bridge. The various ways the four diodes in the bridge circuit are drawn have been shown in Fig. 15.6 (a) and (b). As shown in Fig. 15.6 (a), the arrow head symbols of all the diodes are pointing towards the positive terminal of the output, i.e., the load.



During the positive half cycle of the input voltage, terminal A of the transformer is positive. Current will flow from the positive terminal through diode  $D_1$ , load  $R_L$  and diode  $D_4$ , and back to the negative terminal, B of the transformer. The direction of current through the load has been shown to be from C to D, i.e., from top to bottom. The polarities of the load terminals have been shown. During this period diodes  $D_2$  and  $D_3$  are reverse biased.

During the negative half cycle of the input voltage diodes  $D_3$  and  $D_2$  are forward biased while diodes  $D_1$  and  $D_4$  are reverse biased. Current through the load will flow in the same direction, i.e., from terminal C to D. During both positive and negative half cycles of the input voltage, current will pass through the load in the same direction. The output voltage wave shape is a series of positive half cycles of the sinusoidal voltage. This is dc output but having a varying magnitude. The transformer provides isolation of the dc output from the supply ac input.

The important parameters of a full-wave bridge rectifier are determined as follows.


### 15.1.6 Analysis of Full-Wave Rectifiers

Average value or dc value of load current,  $I_{dc}$ : The average value or dc value will be the same if calculated for a period 0 to  $\pi$  or 0 to  $2\pi$

$$\begin{aligned} I_{dc} &= \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta \, d\theta \\ &= \frac{I_m}{\pi} \int_0^{\pi} \sin \theta \, d\theta \\ &= \frac{I_m}{\pi} [-\cos \theta]_0^{\pi} \\ &= \frac{I_m}{\pi} [ -(-1) - (-1) ] \\ &= \frac{2I_m}{\pi} \end{aligned}$$

RMS value of the load current,  $I_{rms}$

$$\begin{aligned} I_{rms}^2 &= \frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \theta \, d\theta \\ &= \frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) \, d\theta \\ &= \frac{I_m^2}{2\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} \\ &= \frac{I_m^2}{2\pi} \times \pi = \frac{I_m^2}{2} \\ I_{rms} &= \frac{I_m}{\sqrt{2}} \end{aligned}$$

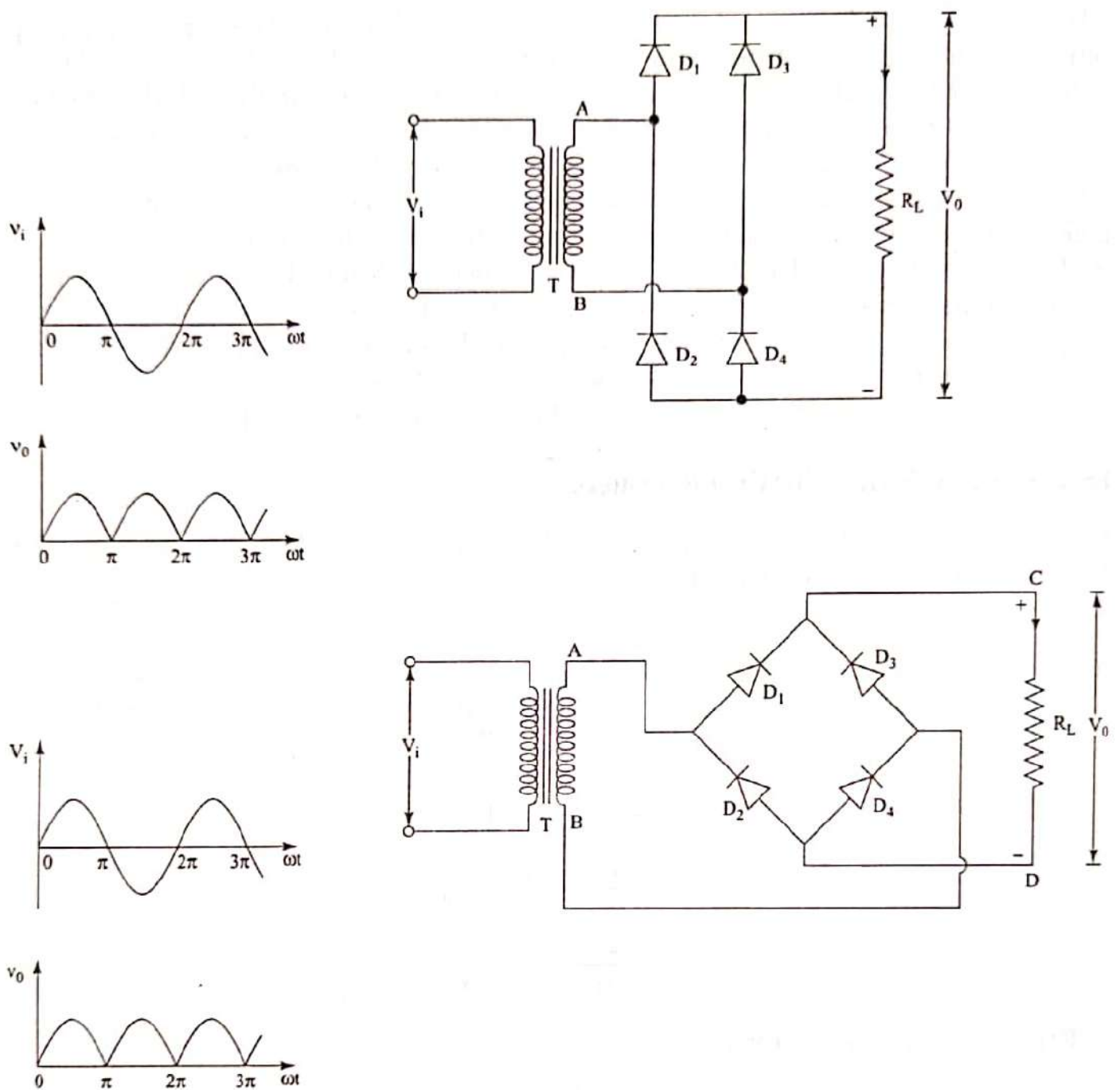**FIGURE 15.6**

A bridge rectifier circuit for full-wave rectification using four diodes and a transformer

Output voltage,  $V_{dc}$

$$\begin{aligned}
 V_{dc} &= I_{dc} R_L \\
 &= \frac{2 I_m}{\pi} R_L \\
 &= \frac{2 R_L}{\pi} \frac{V_m}{(R_L + 2R_F + R_2)}
 \end{aligned}$$



where  $R_L$  is the load resistance,  $R_F$  is the forward resistance of the diode, and  $R_2$  is the secondary winding resistance of the transformer.

Rectifier efficiency,  $\eta$

$$\begin{aligned}
 \eta &= \frac{\text{dc power output, } P_{dc}}{\text{ac power input, } P_{ac}} \\
 &= \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_L + 2R_F + R_2)} \quad (\text{Two diodes being in series}) \\
 &= \frac{(2I_m)^2 R_L}{\pi^2 I_{rms}^2 (R_L + 2R_F + R_2)} \\
 &= \frac{(2\sqrt{2} I_{rms})^2 R_L}{\pi^2 I_{rms}^2 (R_L + 2R_F + R_2)} \\
 &= \frac{8 I_{rms}^2}{\pi^2 I_{rms}^2 \left(1 + \frac{2R_F + R_2}{R_L}\right)} \\
 &= \frac{8}{\pi^2} = 0.812 \quad \text{since } (2R_F + R_2) \ll R_L \\
 &= 81.2 \text{ per cent}
 \end{aligned}$$

Ripple Factor

$$\text{Ripple factor, } r = \frac{\text{RMS value of ac component}}{\text{dc component}}$$

$$= \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

$$\text{Substituting, } I_{rms} = \frac{I_m}{\sqrt{2}} \quad \text{and} \quad I_{dc} = \frac{2I_m}{\pi}$$

$$\begin{aligned}
 r &= \sqrt{\left(\frac{I_m \pi}{\sqrt{2} 2 I_m}\right)^2 - 1} \\
 &= \sqrt{\frac{\pi^2}{8} - 1} \\
 &= 0.48
 \end{aligned}$$

We had earlier calculated the ripple factor for a half-wave rectifier as 1.21. For a full-wave rectifier, the ripple factor is reduced to 0.48. This indicates that the fluctuation of dc output is reduced. PIV for a bridge rectifier =  $V_m$ .

It is now possible to compare the performance parameters of a half-wave rectifier with a bridge rectifier. This has been shown in Table 15.1. Although the performance parameters of

a bridge rectifier are superior than a half-wave rectifier, the quality of output voltage is still not acceptable and has ripple content which must be further minimized. This is achieved by using filters. Filters are discussed in the section that follows.

### 15.1.7 Comparison of Half-Wave and Full-Wave Rectifiers

The performance of half-wave and full-wave rectifiers with respect to certain parameters has been compared as in Table 15.1.

TABLE 15-1	Comparison of Half-wave and Full-wave Rectifiers Against Their Salient Parameters		
Parameters	Half-wave rectifier	Full-wave rectifier with centre-tapped transformer	Bridge rectifier
Number of diodes reqd.	1	2	4
DC load current, $I_{dc}$	$\frac{I_m}{\pi}$	$\frac{2I_m}{\pi}$	$\frac{2I_m}{\pi}$
RMS value or load current $I_{rms}$	$\frac{I_m}{2}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$
DC output, $P_{dc}$	$I_{dc}^2 R_L$ $= \frac{I_m^2}{\pi^2} R_L$	$\frac{4I_m^2}{\pi^2} R_L$	$\frac{4I_m^2}{\pi^2} R_L$
AC input, $P_{ac}$	$I_{rms}^2 (R_L + R_F + R_2)$ $= \frac{I_m^2}{4} (R_L + R_F + R_2)$	$I_{rms}^2 (R_L + 2R_F + R_2)$ $= \frac{I_m^2}{2} (R_L + 2R_F + R_2)$	$I_{rms}^2 (R_L + 2R_F + R_2)$ $= \frac{I_m^2}{2} (R_L + 2R_F + R_2)$
Maximum rectification efficiency	40%	81.2%	81.2%
Ripple factor	1.21	0.48	0.48
PIV	$V_m$	$2 V_m$	$V_m$

(continued)



**TABLE 15-1** Comparison of Half-wave and Full-wave Rectifiers Against Their Salient Parameters (continued)

Parameters	Half-wave rectifier	Full-wave rectifier with centre-tapped transformer	Bridge rectifier
Ripple frequency	$Fr = f$	$Fr = 2f$	$Fr = 2f$
Centre tap transformer	Not required	Required	Not required
Transformer utilization factor	28.7%	69.2%	81.2%

### EXAMPLE 15.4

The input to a bridge rectifier is through a step-down transformer of turn ratio 10:1. The supply voltage is 230 V at 50 Hz. The load resistance is 1.2 k $\Omega$  secondary winding resistance of the transformer is 4  $\Omega$  diode forward resistance is 2  $\Omega$ . Calculate the efficiency of the bridge rectifier.

#### SOLUTION

Given  $V_i$  (RMS) = 230 V


$R_F = 2 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_L = 1200 \Omega$

The RMS value of the emf in transformer secondary

$$\begin{aligned}
 V_s \text{ (RMS)} &= 230 \left( \frac{N_2}{N_1} \right) \\
 &= 230 \left( \frac{1}{10} \right) \\
 &= 23 \text{ V}
 \end{aligned}$$

Peak secondary voltage,  $V_m$  is

$$\begin{aligned}
 V_m &= \sqrt{2} V_s \text{ (RMS)} \\
 &= \sqrt{2} \times 23 \\
 &= 32.5 \text{ V}
 \end{aligned}$$

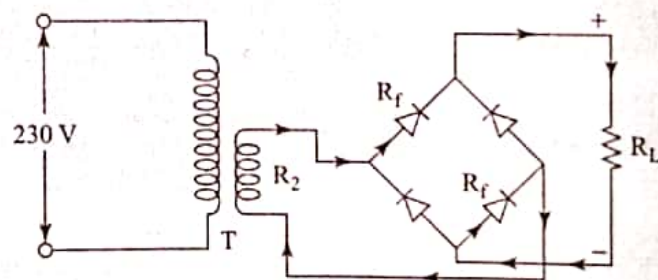

**FIGURE 15.7**

Bridge-rectifier circuit

Current through the load will flow from the transformer secondary via two diodes. Therefore, following the current path during the positive half cycle

$$I_m = \frac{V_m}{R_L + 2R_F + R_s} = \frac{32.5}{1200 + 4 + 4} = 26.8 \text{ mA}$$

For a bridge rectifier,

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 26.8}{3.14} = 17 \text{ mA}$$

$$\begin{aligned} \text{DC power output, } P_{dc} &= I_{dc}^2 R_L = (17 \times 10^{-3})^2 \times 1200 \\ &= 346.8 \text{ mW} \end{aligned}$$

$$\begin{aligned} \text{AC power input, } P_{ac} &= (I_{rms})^2 (R_L + 2R_F + R_s) \\ &= \left( \frac{I_m}{\sqrt{2}} \right)^2 (R_L + 2R_F + R_s) \\ &= \left( \frac{26.8 \times 10^{-3}}{2} \right)^2 \times (1200 + 2 \times 2 + 4) \\ &= 432 \text{ mW} \end{aligned}$$

$$\text{Rectifier efficiency, } \eta = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{346.8 \times 100}{432} = 80 \text{ per cent.}$$

### EXAMPLE 15.5


Determine for the bridge circuit shown in Fig. 15.8, the peak value of load current when  $V_i = 15 \text{ V}$ ,  $R_L = 600 \Omega$  and the forward voltage drop of the diode is  $0.7 \text{ V}$ . Also calculate the average value of the output current

#### SOLUTION

$$\begin{aligned} V_i &= 15 \text{ V} \\ V_i(\text{max}) &= \sqrt{2} \times 15 = 21.21 \text{ V} \end{aligned}$$

Maximum value of voltage appearing across the load will be  $V_i(\text{max}) - 2V_F$ .

This is because two diodes are involved in the current flow through the load at any point of time

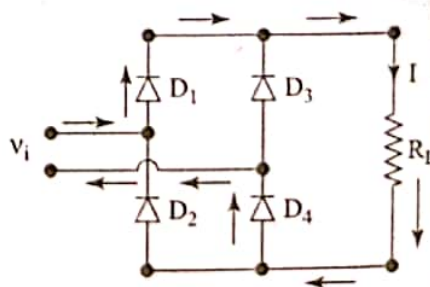

**FIGURE 15.8**

Bridge rectifier circuit



$$\begin{aligned}
 V_o(\max) &= V_i(\max) - 2 V_F \\
 &= 21.21 - 2 \times 0.7 \\
 &= 19.81 \text{ V}
 \end{aligned}$$

$$I_o(\max) = \frac{V_o(\max)}{R_L} = \frac{19.81}{600} = 36 \text{ mA}$$


$$I_o(\text{average}) = I_{dc} = \frac{2 I_m}{\pi} = \frac{2 \times 36}{3.14} = 22.93 \text{ mA}$$

## 15.2 ► FILTERS

We have seen that the wave form of the rectified voltage is a series of positive half cycles of the input voltage wave form either of equal or of reduced magnitude. For a half-wave rectifier we get a series of positive half cycles with one missing in between. Our objective is to get a steady-value dc output. To convert the fluctuating output voltage into a steady dc, smoothing circuits called filters must be used. The simplest filter is a capacitor which is connected across the load. Fig. 15.9 shows a capacitor  $C$  connected across the load resistance  $R_L$  in a half-wave rectifier. The effect of the use of a capacitor on the output voltage wave has been shown.

During the positive half cycle of the input voltage the diode  $D_1$  is forward biased. Current flows through the diode and the load resistor,  $R_L$ . At the same time the capacitor,  $C$  gets charged upto the peak value,  $V_m$  of the input voltage.

After attaining the pick value, the input voltage starts reducing, its value becoming less and less than  $V_m$ . But the capacitor has been charged to a voltage  $V_m$ . Thus, the potential of terminal B becomes higher than the potential of terminal A. As a result, diode  $D_1$  gets reverse biased but the capacitor voltage remains close to  $V_m$ . With the diode  $D_1$  reverse biased, the changing of the capacitor stops. The capacitor now starts getting discharged through the load resistor  $R_L$ . The voltage across the capacitor,  $V_C$  starts falling, as has been shown in Fig. 15.9, through a thick horizontally inclined line. The diode,  $D_1$  remains reverse biased throughout the rest of the positive half cycle and also during the negative half cycle, and further to the next positive half cycle until at  $\theta_2$  when the input voltage starts becoming higher than the capacitor voltage,  $V_C$  once again. At this point the

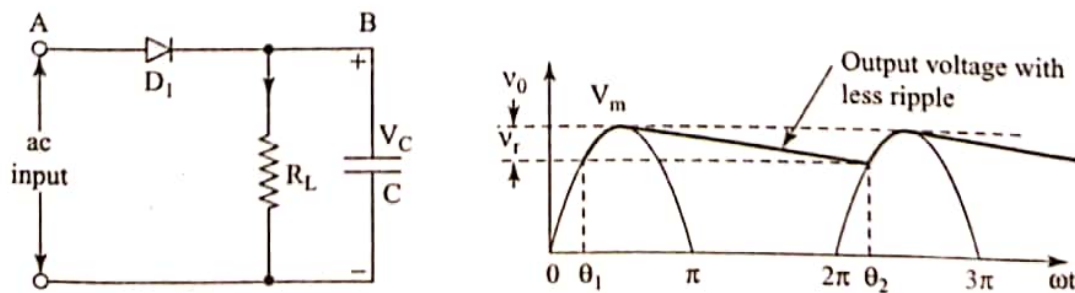


**FIGURE 15.9**

Half-wave rectifier circuit with a capacitor filter

diode becomes conducting supplying current to the load as also charging the capacitor once again. This process of charging and discharging of the capacitor continues in every cycle and an output voltage waveform, as shown by a thick line, is achieved. This wave shape of the output voltage is superior to the wave shape of the output voltage obtained when no capacitor was connected. The ripple of the output voltage is now reduced and a near-steady dc output voltage obtained.

### Amplitude of ripple voltage and selection of capacitor

The half-wave rectified voltage with a capacitor filter has been shown again in Fig. 15.10.  $V_r$  represents the peak to peak ripple voltage. The time of discharge of the capacitor is represented by  $t_1$  as shown in Fig. 15.10. The output voltage fluctuates between  $V_0$  (min) to  $V_0$  (max).

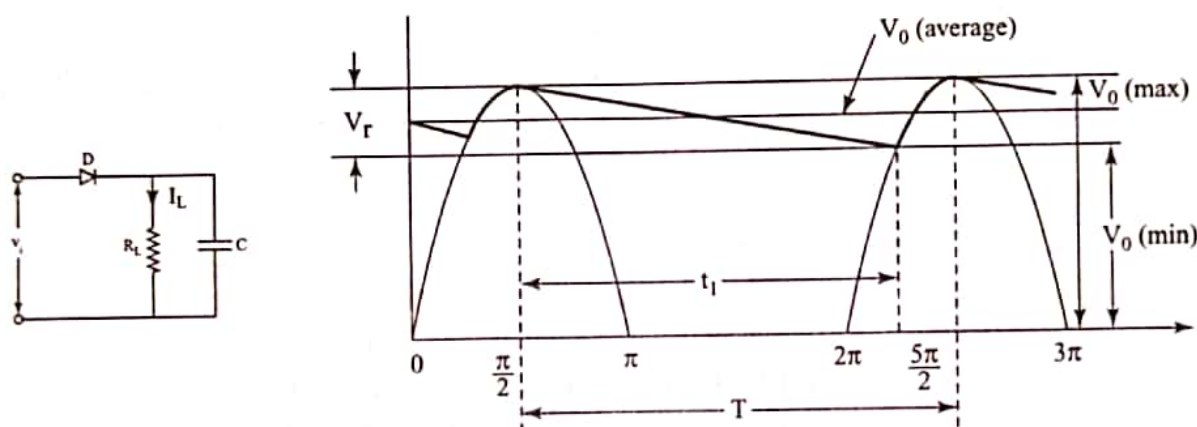

**FIGURE 15.10**

Half-wave rectified voltage with a capacitor filter

Peak to peak,  $V_r = V_0(\text{max}) - V_0(\text{min})$ .

Average value of output voltage,  $V_0(\text{average}) = \frac{V_0(\text{max}) + V_0(\text{min})}{2}$

The capacitor  $C$  gets discharged during the time  $t_1$  when the voltage across it drops by  $V_r$ , causing a load current,  $I_L$  to flow through the resistance  $R_L$ . So we can write

$$Q = CV_r = I_L \times t$$

or,

$$C = \frac{I_L \times t}{V_r} \quad (i)$$

Calculation of the value of the capacitor to be used depends on the allowable ripple voltage, the average output voltage, the load resistance, and the supply frequency. The approximate value is calculated using the procedure illustrated through an example. The standard manufacture's list is then consulted to select the next higher value of the capacitor available in the market.




**EXAMPLE 15.6**

A half-wave capacitor filter rectifier has maintained an average output voltage of 15 V with a peak to peak ripple of not more than 3 V. The load resistance is  $100\ \Omega$ . Calculate the value of the capacitor filter. The ac supply frequency is 50 Hz.

**SOLUTION**

$$\begin{aligned}\text{The load current, } I_L &= \frac{V_o(\text{average})}{R_L} \\ &= \frac{15}{100} \text{ A} = 150 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{Time period, } T &= \frac{1}{f} = \frac{1}{50} \text{ seconds} \\ &= \frac{1000}{50} \text{ ms} = 20 \text{ ms}\end{aligned}$$

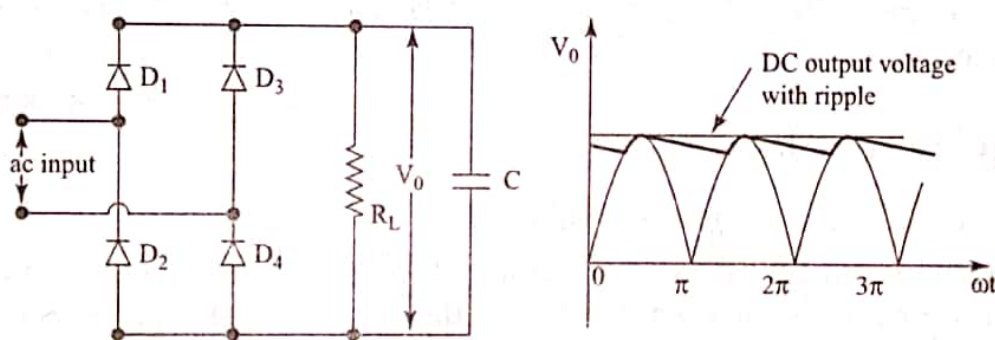**FIGURE 15.11**

Bridge rectifier with a smoothing capacitor

The time of discharge of the capacitor  $t_1$  can approximately be considered equal to  $T$ . Therefore,

$$t_1 = T = 20 \text{ ms}$$

using the relation,

$$\begin{aligned}CV_r &= I_L t_1 \\ C &= \frac{I_L t_1}{V_r} = \frac{150 \times 10^{-3} \times 20 \times 10^{-3}}{3} = 1000 \mu\text{F}\end{aligned}$$

Capacitors of  $100\ \mu\text{F}$  are available as can be checked from the manufacturer's list.

Similar to the capacitor filter used in half-wave rectifiers, capacitor filters are used in full-wave rectifier also as shown in Fig. 15.11. The circuit works exactly the same way as has been explained in the case of half-wave rectifier with a capacitor filter. From the dc output voltage wave shape it is observed that the ripple is minimized to a very small level.

The ripple voltage that appears across the capacitor can further be reduced by use of another resistor and a capacitor. The resistor is connected in series while the capacitors