




### MID TERM EXAMINATIONS – October-November 2023

Programme	: B.Tech.	Semester	: Fall 2023-24
Course Title/ Course Code	: Electric Circuits and Systems/ EEE1001	Slot	: E11+E12+E14
Time	: 1 ½ hours	Max. Marks	: 50

Answer all the Questions


Q.No.	Sub. Sec.	Question Description	Marks
-------	-----------	----------------------	-------

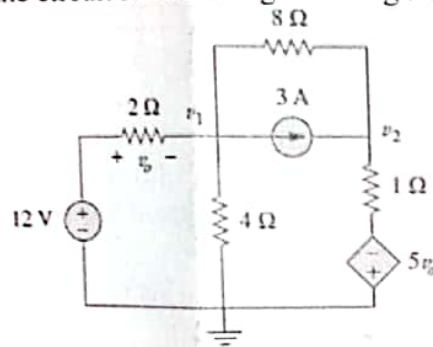- 1 a Determine the  $v_1$  and  $v_2$  in the circuit shown in figure using nodal analysis.




6

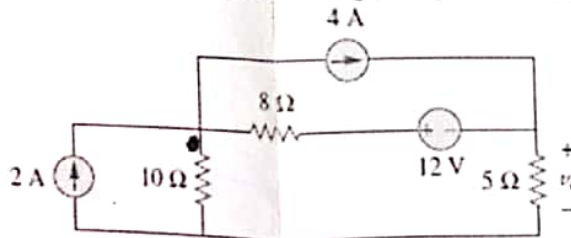- b Using superposition theorem, determine the voltage drop  $v_o$  across the  $5\Omega$  resistor.




4

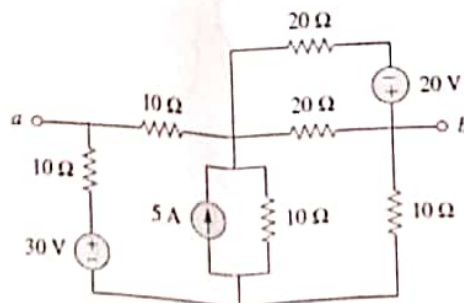- 2 a For the circuit shown in figure, find the Thevenin's equivalent circuit between the terminals a & b.




5

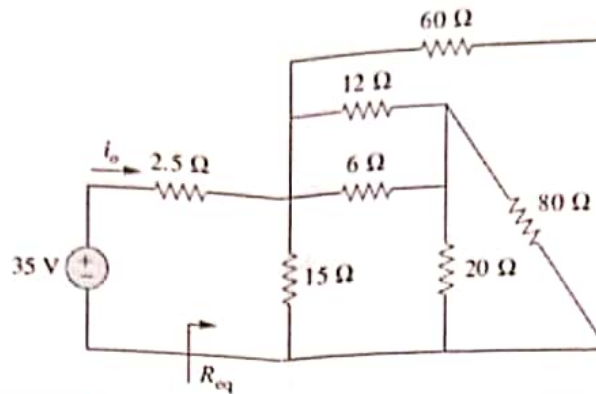- b Determine the equivalent resistance for the circuit shown below and find the current  $i_0$  flowing through  $2.5\Omega$  resistor.



5

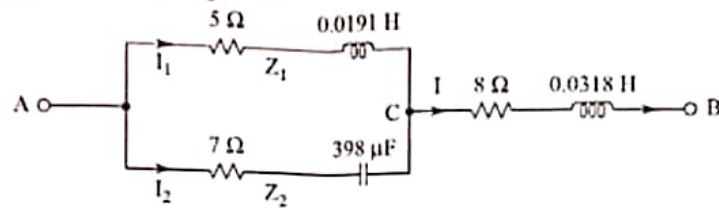- 3 a In the circuit shown in figure determine the voltage at 50 Hz to be applied across terminals AB in order that a current of 10A flows in the capacitor ( $398\mu F$ ). Draw the phasor diagram for the circuit given.



6


- b A circuit of  $R=4\Omega$ ,  $L=0.5H$  and a variable capacitance  $C$  in series is connected across a 100V, 50 Hz supply. Calculate: (a) the value of the capacitance for which resonance will occur; (b) the voltage across the capacitor at resonance and the Q-factor of the circuit.

4

- 4 (a) A linear inverse continuous system is specified by  $\frac{d^2y(t)}{dt^2} - 7\frac{dy(t)}{dt} + 10y(t) = \frac{dx(t)}{dt} + 5x(t)$  the input is  $x(t) = e^{-5t}u(t)$ . Find the (i) natural response for the initial condition,  $y(0^+) = 6$ ,  $\frac{dy(0^+)}{dt} = 0$  (ii) forced response and (iii) total response of the system.

6

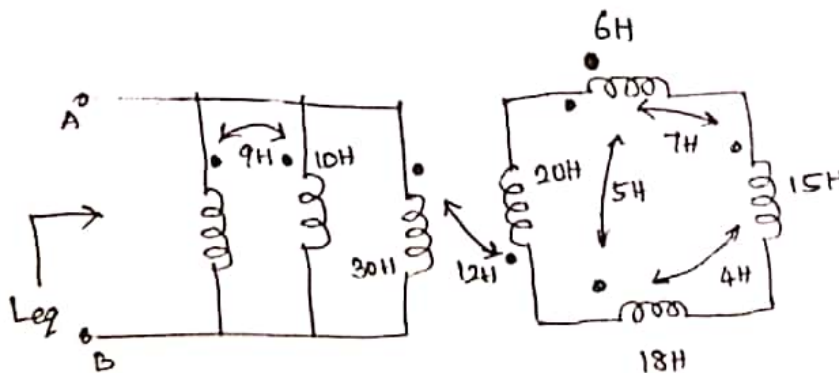
- (b) Determine the equivalent inductance for the mutual coupled circuit shown in figure.



4

- 5 Interpret the working of p-n junction diode at different bias conditions with its V-I characteristics. In regard to the characteristics of the p-n junction diode, its forward characteristics is shown below. Find the dc forward resistance at point P and dynamic forward resistance.

10

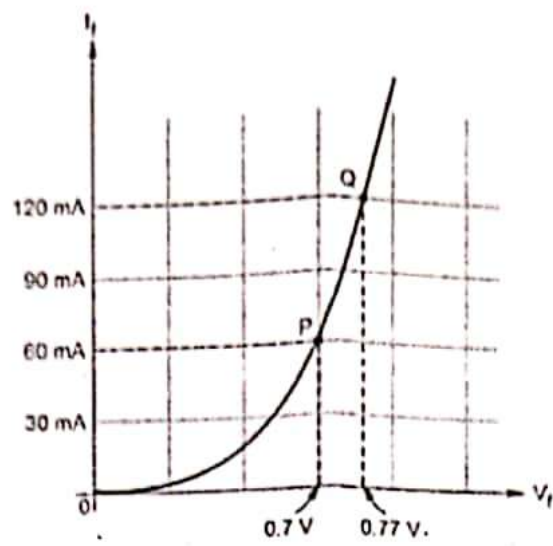

⇒⇒⇒