

Reg. No.:

Name :


**VIT<sup>®</sup>**  
**BHOPAL**

www.vitbhopal.ac.in

**MID TERM EXAMINATIONS – October-November 2023**

Programme	: B.Tech.	Semester	: Fall 2023
Course Title/ Course Code	: Electric Circuits and Systems/ EEE1001	Slot	: C11+C12+C13
Time	: 1 ½ hours	Max. Marks	: 50

**Answer all the Questions**

Q.No.	Sub. Sec.	Question Description	Marks
-------	--------------	----------------------	-------

- 1 Find the current through each of the sources and their power dissipation in the network shown in Fig. 1 by identifying a suitable technique on your own.

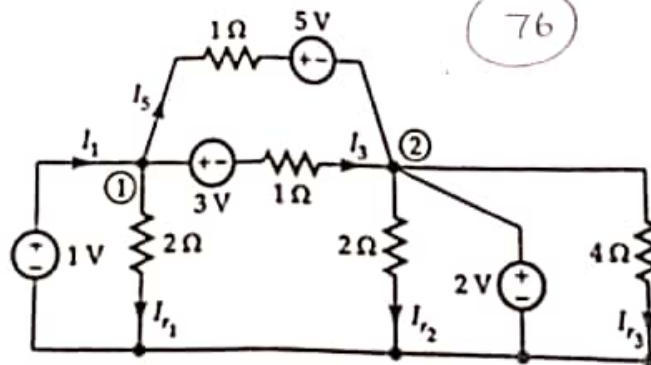


Fig.1

10

- 2 a) Find the current through  $r_L$  using Thevenin's theorem for the circuit shown in Fig.2

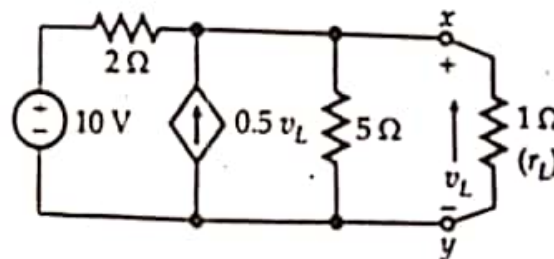


Fig. 2

5

- 2 (b) Calculate the amount of maximum power transfer to  $R$  in the circuit shown in Fig.3

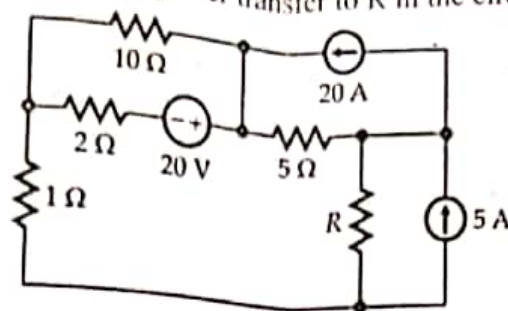


Fig.3

- 3 (a) A choke coil is connected across a 250 V, 50 Hz supply. If the input current be 10 A and power loss in the choke be 1 kW, find the impedance, resistance and inductance of the choke.

What is the power factor of the circuit?

What would be the value of input current if a capacitor of  $C$  Farad is connected in series with the coil and such that the power factor of the entire circuit becomes unity.

- 3 (b) Consider a series RLC circuit, in which the maximum inductor voltage is twice the capacitor voltage maximum. However, the circuit current lags the applied voltage by  $30^\circ$  and the instantaneous drop across the inductance is given by  $v_L = 200 \sin 377 t$  V. Assuming the resistance being  $40 \Omega$ , find the values of inductance and capacitance.

- 4 Consider a linear time inverse continuous system given by  

$$\frac{d^2 y(t)}{dt^2} + 9 \frac{dy(t)}{dt} + 14y(t) = \frac{dx(t)}{dt} + 3x(t)$$
the input is  
 $x(t) = e^{-t} u(t).$

Find (i) Natural response for initial condition  $y(0^+) = 5, \frac{dy(0^+)}{dt} = 0$

(ii) Forced response and (iii) Total response.

- 5 (a) A full-wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at  $20 \Omega$ . The transformer r.m.s. secondary voltage from centre tap to each end of secondary is 50 V and load resistance is  $980 \Omega$ . Find : (i) the mean load current (ii) the r.m.s. value of load current.

- 5 (b) A half-wave rectifier is used to supply 50V d.c. to a resistive load of  $800 \Omega$ . The diode has a resistance of  $25 \Omega$ . Calculate a.c. voltage required.

